

Name: O G RAGAVI

Register no: 20BCE1988

Date: 1-09-2022

Experiment No.4


Verification of Thevenin's theorem

Objective:

To design a simplified equivalent circuit in analysing the power systems and other circuits where the load resistor is subject to change in order to determine the voltage across it and current through it using Thevenin's theorem.


Statement of the theorem:

Any two-terminal linear network composed of voltage sources, current sources, and resistors, can be replaced by an equivalent two-terminal network consisting of an independent voltage source in series with a resistor. The value of voltage source is equivalent to the open circuit voltage (V_{th}) across two terminals of the network and the resistance is equal to the equivalent resistance (R_{th}) measured between the terminals with all energy sources replaced by their internal resistances.

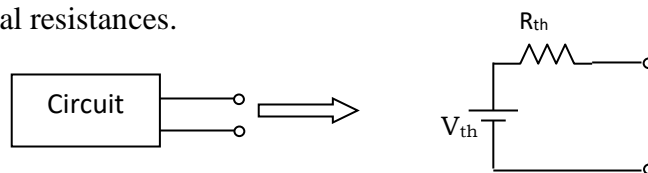

I.Simulation results

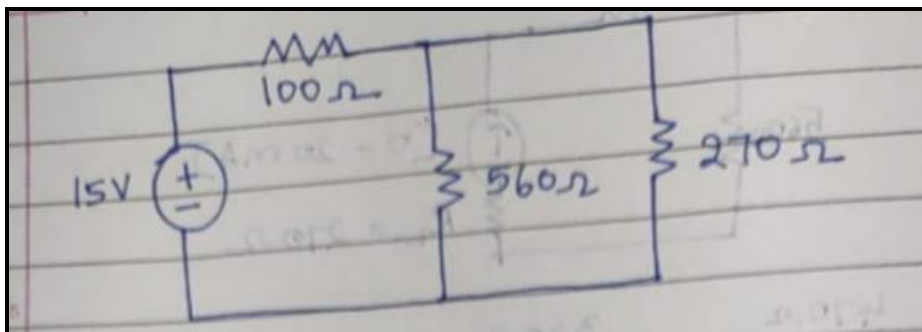
1. Include your theoretical Circuit diagram here:




2. Theoretical calculation:

Theoretical calculation:


Finding V_{th} :

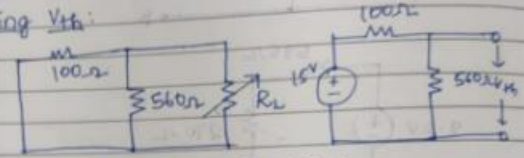
$$R_{th} = 100 \parallel 560 = 84.85 \Omega$$
$$V_{th} = \left(\frac{560}{560 + 100} \right) \times 16$$
$$= 12.73V$$


Thevenin Equivalent Circuit:

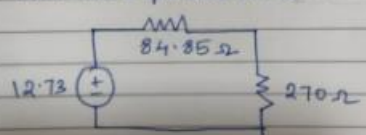
$$I_x = \frac{V_{th}}{R_{th} + R_L} = \frac{12.73}{84.85 + 270} = 0.036A$$

Finding R_{th} :

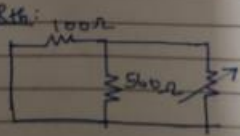
$$R_{th} = 100 \parallel 560 = 84.85 \Omega$$

3. Simulation:

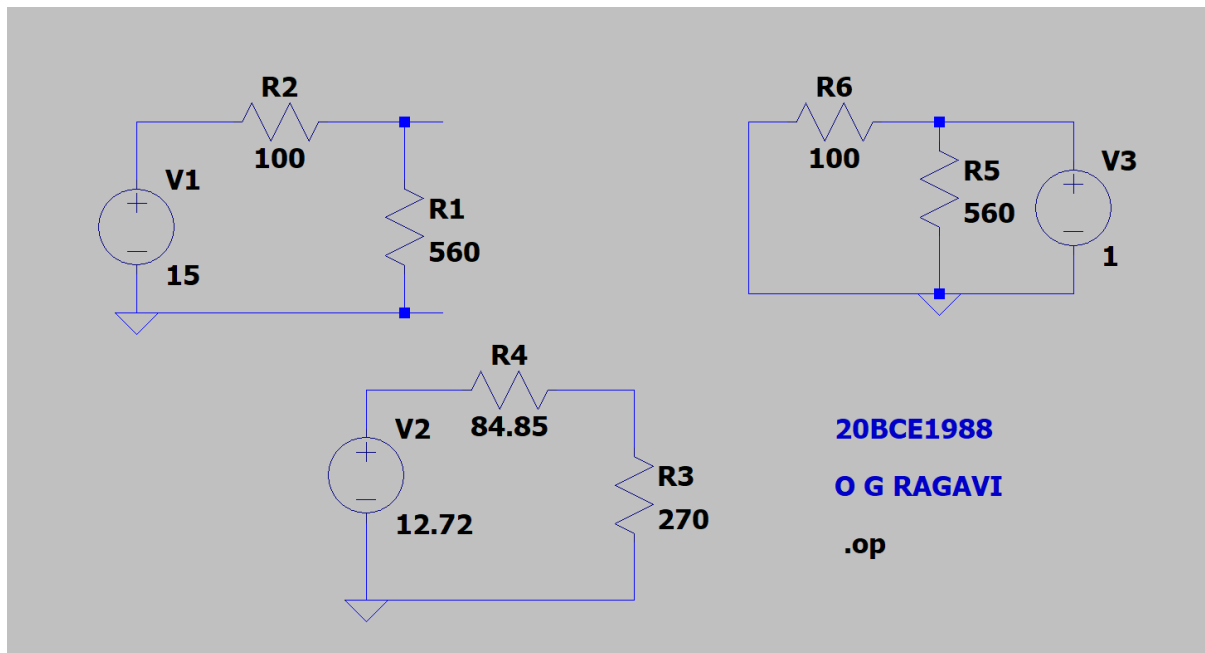

* C:\Users\ragav\OneDrive\Documents\LTspiceXVII\Draft2.asc


```

--- Operating Point ---
V(n001):      15          voltage
V(n002):      12.7273     voltage
V(n004):      12.72       voltage
V(n005):      9.67846     voltage
V(n003):      1           voltage
I(R6):        0.01        device_current
I(R5):        0.00178571  device_current
I(R4):        -0.0358461  device_current
I(R3):        0.0358461   device_current
I(R2):        -0.0227273  device_current
I(R1):        0.0227273   device_current
I(V3):        -0.0117857  device_current
I(V2):        -0.0358461  device_current
I(V1):        -0.0227273  device_current


```

II. Hardware Experiment results

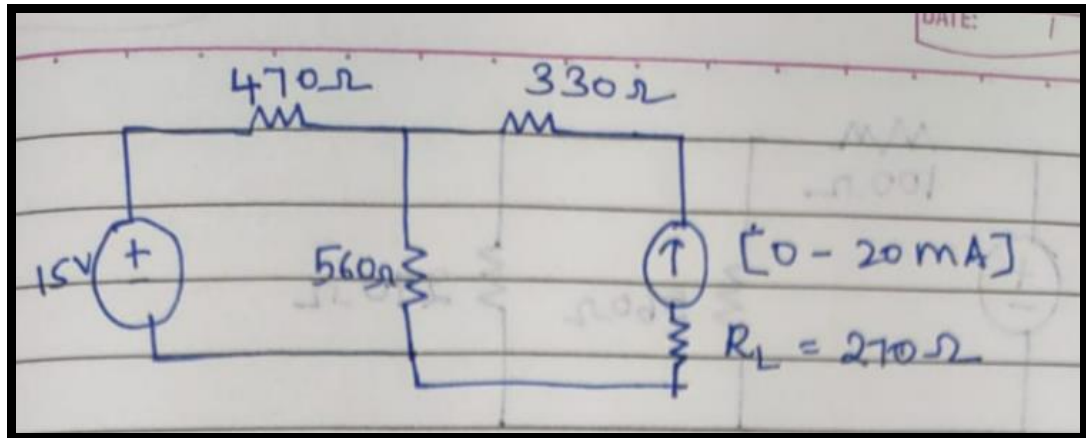
1. Include your theoretical Circuit diagram here:



2. Theoretical calculation:

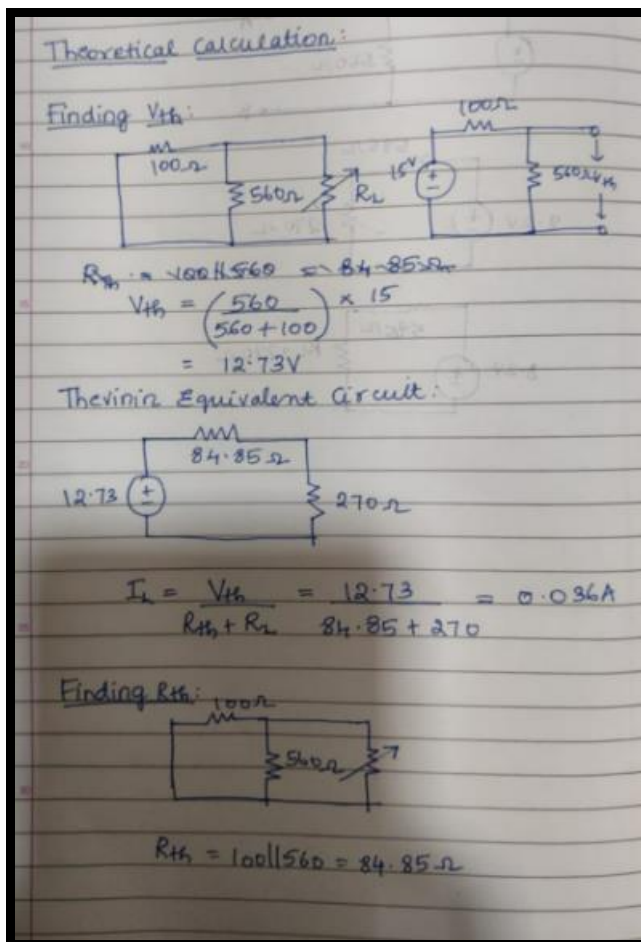

3. Experiment:

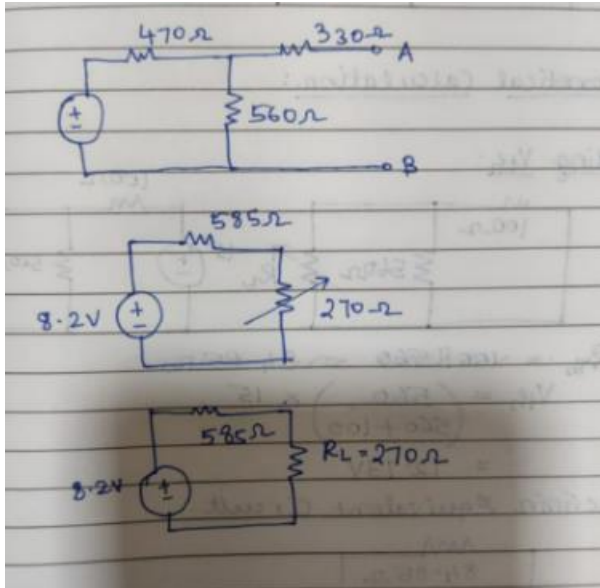

Result:

Thus Thevenin's theorem has been verified both by simulation and experimentation.