

Basic Electrical and electronic Engineering (EEE1001)

NAME: O G Ragavi

REG.NO: 20BCE1988

LAB EX: 2


TITLE: Verification of Kirchhoff's Voltage law

Aim:

To verify Kirchhoff's voltage law by Simulation by using LT spice simulation and by conducting experiment.

Theory:

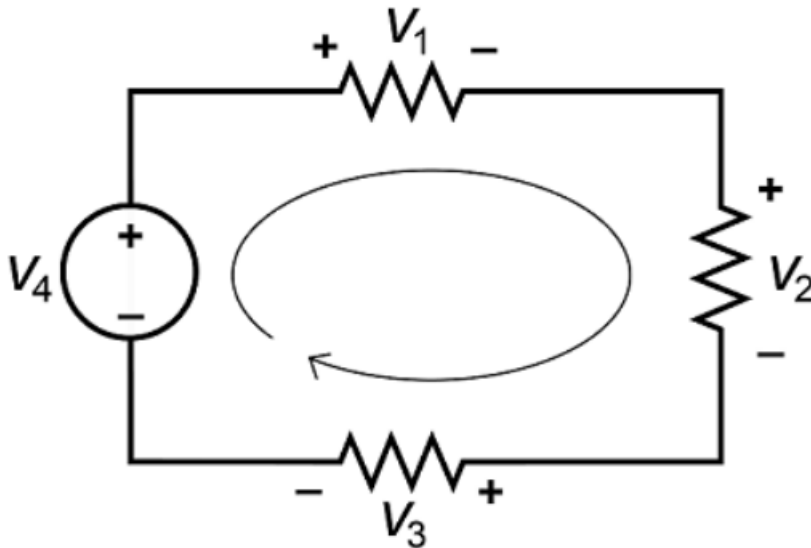Kirchhoff's voltage law states that the algebraic sum of all the potential differences around a closed network must be equal to zero.




Formula:

$$V_1 + V_2 + V_3 - V_4 = 0, \text{ or } V_1 + V_2 + V_3 = V_4.$$

I. Simulation verification

Circuit Diagram:

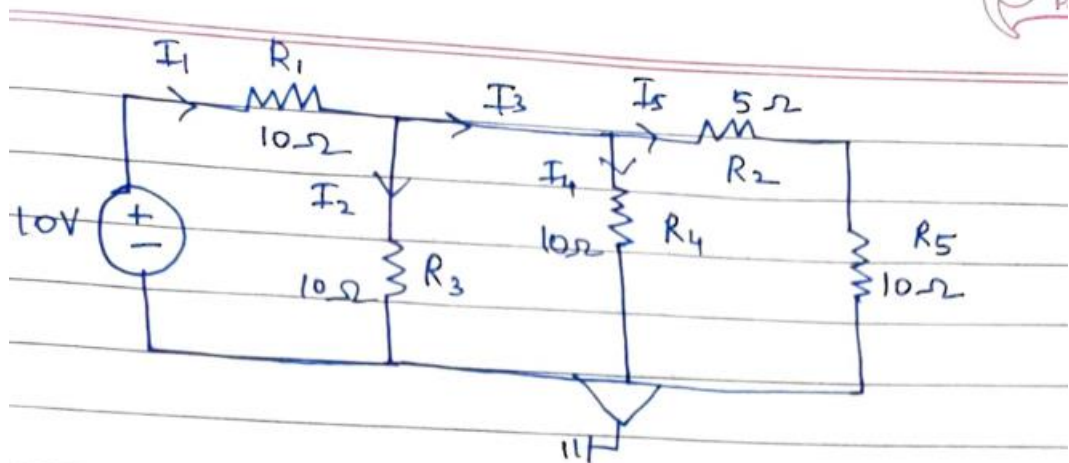

Theoretical calculation:

Theoretical calculation:

Resistance:

$$Req_1 = R_2 + R_5 = 5 + 10 = 15\Omega$$

$$Req_2 = Req_1 \parallel R_4 = 15\Omega \parallel 10\Omega$$

$$\Rightarrow \frac{15 \times 10}{15 + 10} = \frac{150}{25} = 6\Omega$$

$$Req_3 = Req_2 \parallel R_3 = 6\Omega \parallel 10\Omega$$

$$\Rightarrow \frac{6 \times 10}{6 + 10} = \frac{60}{16} = 3.75\Omega$$

$$Req_4 = R_1 + Req_3$$

$$= 10 + 3.75$$

$$= 13.75\Omega$$

$$\therefore \boxed{Req = 13.75\Omega}$$

Current:

$$I_1 = \frac{V}{R_{eq}} = \frac{10}{12.5} = 0.8A$$

$$I_2 = 0.8 \times \frac{6}{16} = 0.3A$$

$$I_3 = 0.8 \times \frac{10}{16} = 0.5A$$

$$I_4 = 0.5 \times \frac{15}{25} = 0.3A$$


$$I_5 = 0.5 \times \frac{10}{25} = 0.2A$$

$$\therefore V_1 = I_1 \times R_1 = 10V$$

$$\therefore V_2 = I_3 \times R_2 = 0.3 \times 10 = 3V$$

$$V_4 = 10V ; V_5 = 3.33V ; V_6 = 6.67V$$

Simulation diagram:

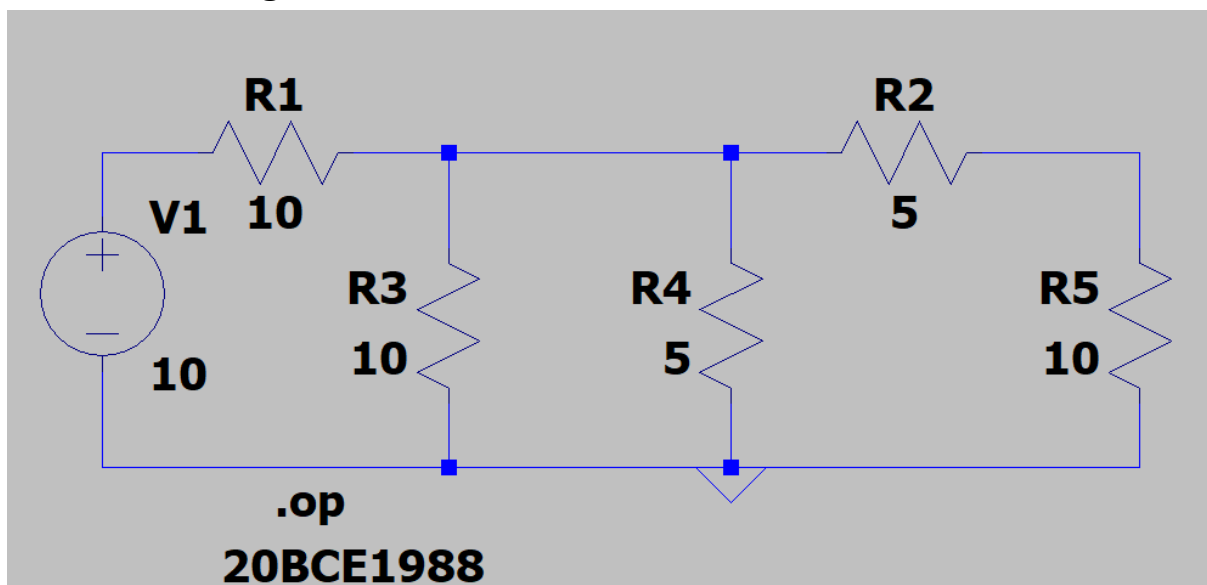

Simulation Result:


* C:\Users\ragav\OneDrive\Documents\LTspiceXVII\Draft1.asc

--- Operating Point ---

V(n001) :	10	voltage
V(n002) :	2.14286	voltage
V(n003) :	1.42857	voltage
I(R5) :	-0.142857	device_current
I(R4) :	-0.428571	device_current
I(R3) :	-0.214286	device_current
I(R2) :	-0.142857	device_current
I(R1) :	-0.785714	device_current
I(V1) :	-0.785714	device_current

2.Experiment

Circuit Diagram:

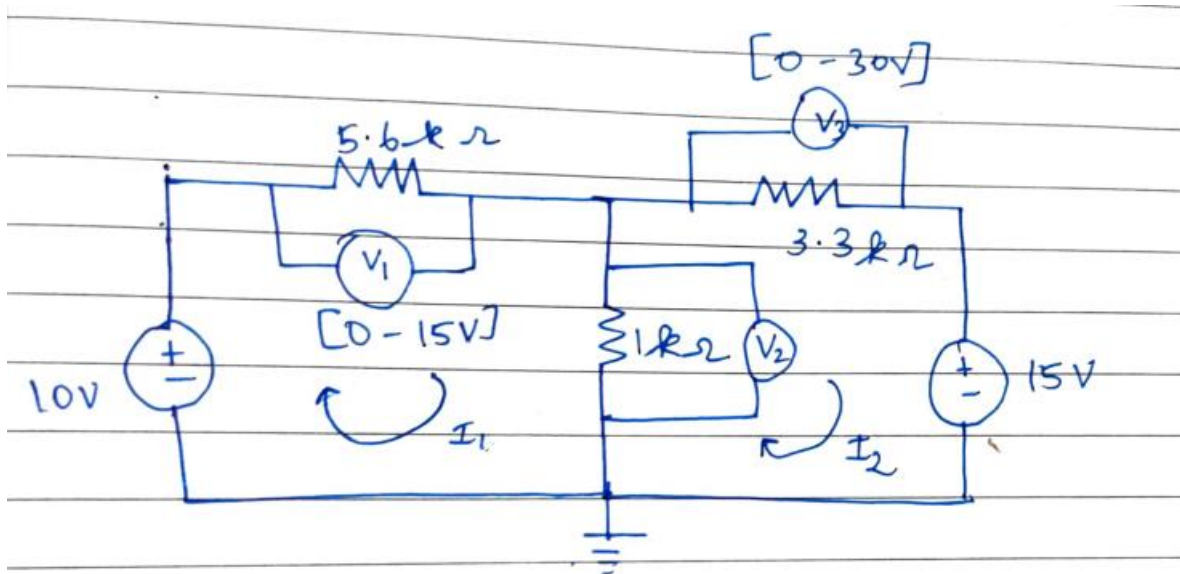

Theoretical calculation:

Theoretical calculation:

$$5.6kI_1 + 1k(I_1 - I_2) = 10V$$

$$3.3kI_2 + 1k(I_2 - I_1) = -15V$$

$$\Rightarrow 6.6kI_1 - 1kI_2 = 10V \rightarrow \textcircled{1}$$

$$-1kI_1 + 4.3kI_2 = -15V \rightarrow \textcircled{2}$$

$$\textcircled{2} \times 6.6 \Rightarrow \textcircled{4}$$

$$\Rightarrow 6.6kI_1 - 1kI_2 = 10V$$

$$-6.6kI_1 + 28.38kI_2 = -99V$$

$$\underline{\underline{27.38kI_2 = -89V}}$$

$$\therefore \boxed{I_2 = -3.251mA}$$

$$I_1 = \frac{10 + 1kI_2}{6.6k} = \frac{10 - 3.251}{6.6 \times 10^{-3}}$$

$$= 1.023mA$$



$$\therefore \boxed{I_1 = 1.023mA}$$

$$\Rightarrow V_1 = 5.6kI_1 = 5.73V$$

$$V_2 = 1k(I_1 - I_2) = 1k \times 4.273mA = 4.27V$$

Experiment Result:

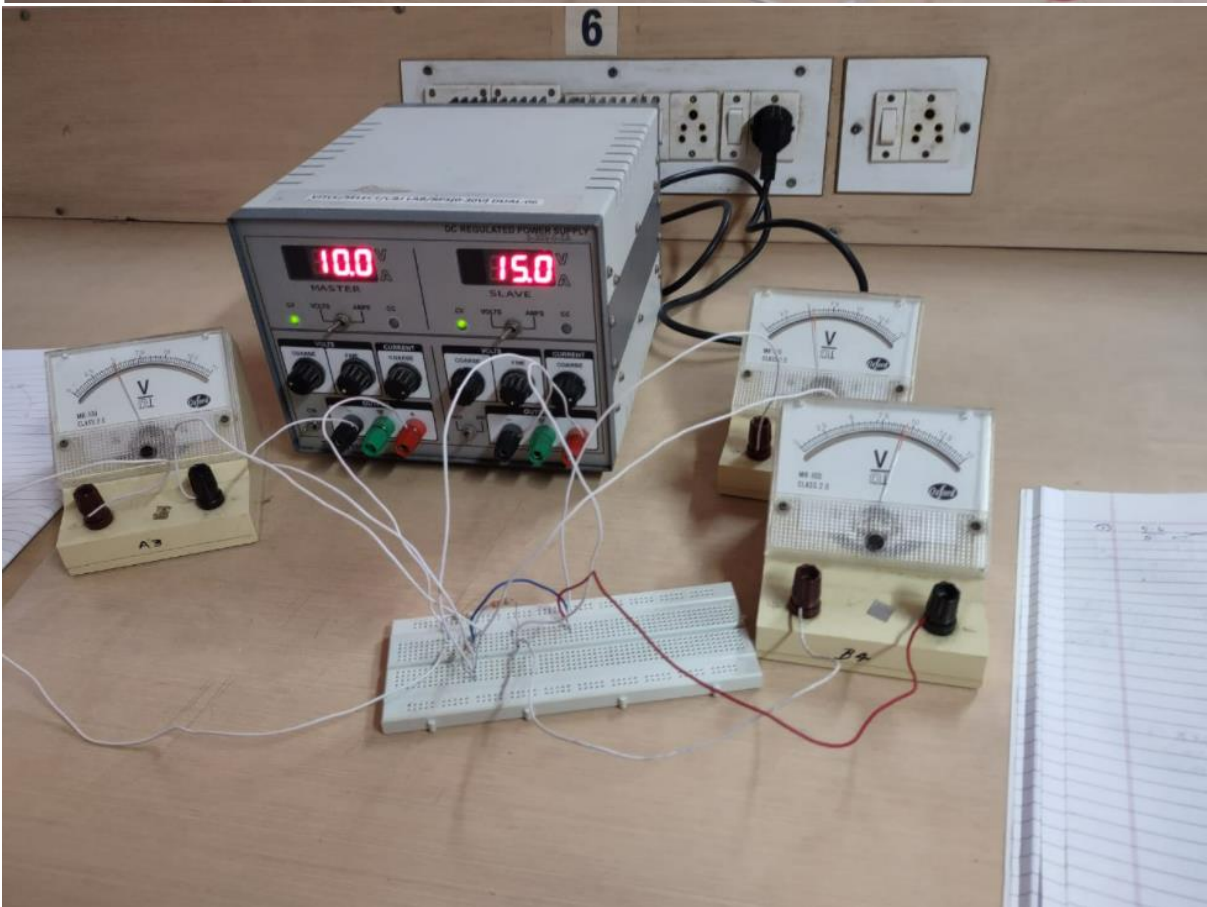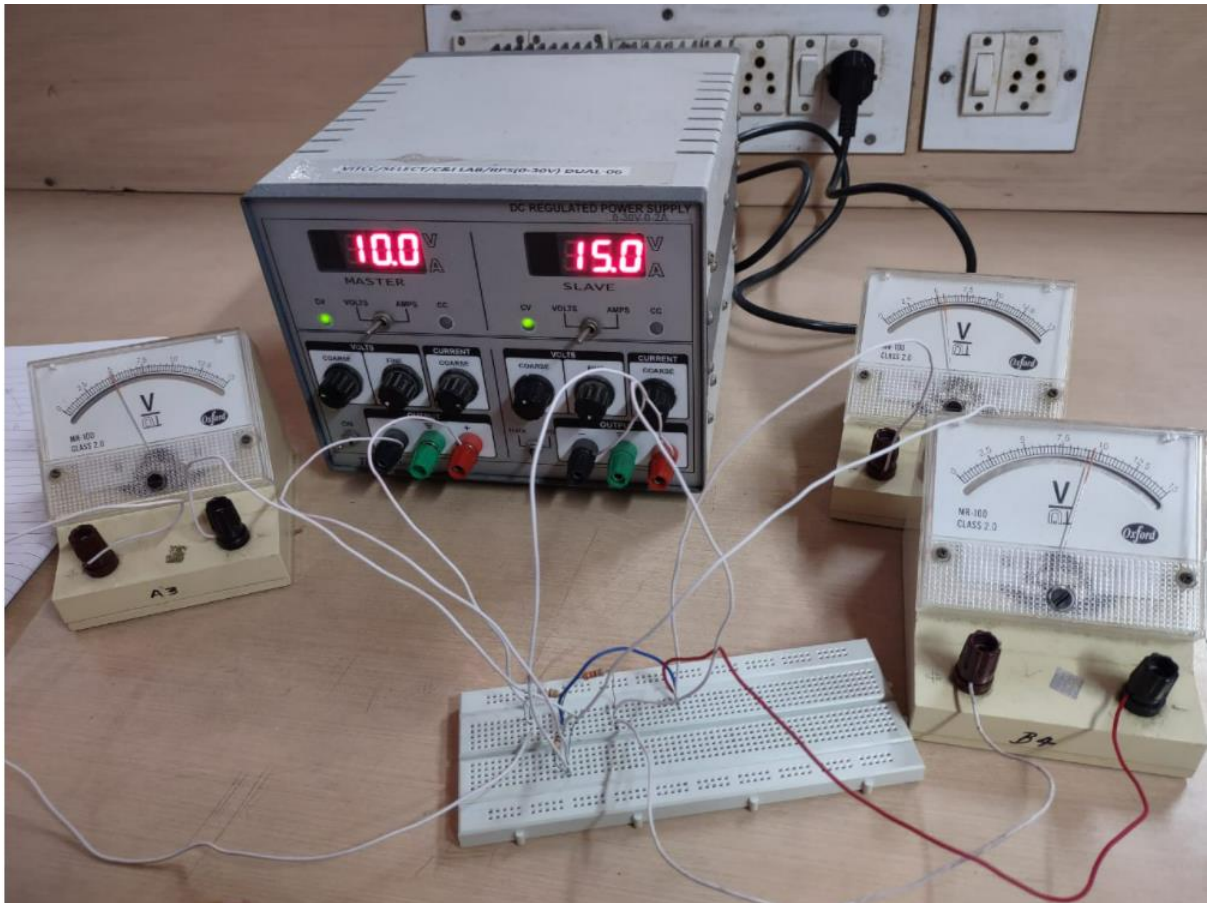The voltages calculated manually in the experiment matched the voltages observed.



Result:

The Kirchhoff's voltage law is verified using LTSpice.