

Measurement of Power in a single-phase AC load

Aim:

To measure the single-phase power in a single phase a.c. circuit by using three voltmeters.

Software Required:

LTspice Software

Circuit Diagram:

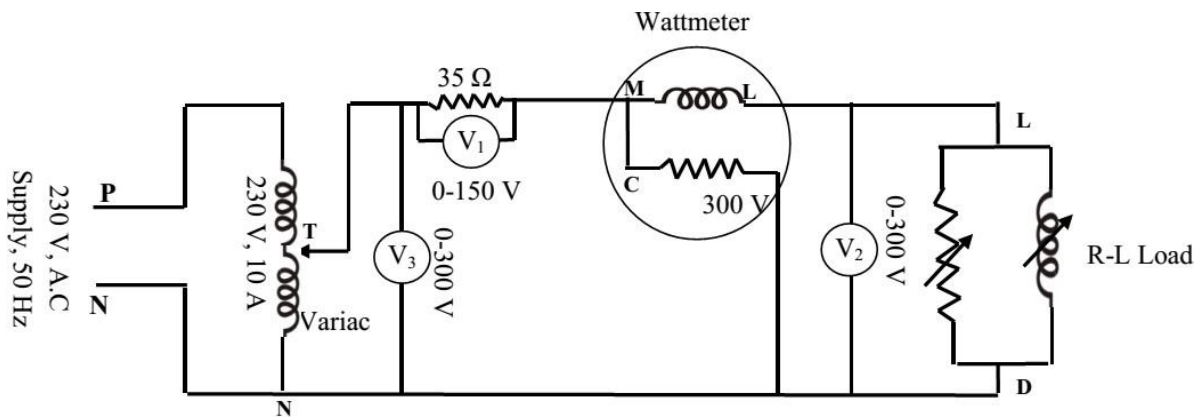


Fig. 1: Circuit Diagram

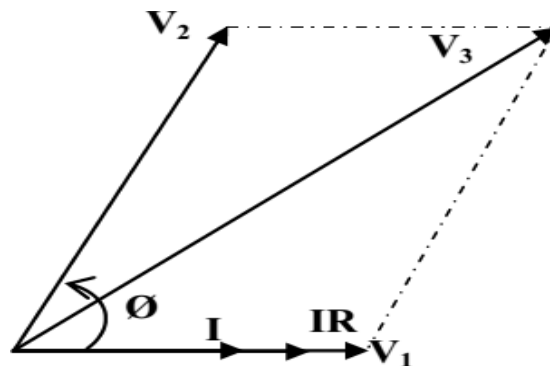


Fig. 2: Phasor Diagram

Theory:

$$\text{Power consumed by load} = P = V_2 I \cos \phi \quad (1)$$

From the phasor diagram we can write,

$$V_3^2 = V_1^2 + V_2^2 + 2 \cdot V_1 \cdot V_2 \cos \phi \quad (2)$$

$$\text{Power factor, } \cos \phi = (V_3^2 - V_1^2 - V_2^2) / 2 \cdot V_1 \cdot V_2 \quad (3)$$


$$I = V_1 / R \quad (\text{Here } R = 35 \text{ Ohm})$$

Now,


$$\begin{aligned} P_{\text{calculated}} &= V_2 I \cos \phi = V_2 (V_1 / R) \cos \phi \\ &= (V_1 V_2 / R) ((V_3^2 - V_1^2 - V_2^2) / 2 \cdot V_1 \cdot V_2) = (1/2R) * (V_3^2 - V_1^2 - V_2^2) \end{aligned} \quad (4)$$

From the above equation it can be observed that, the power and power factor in an a.c circuit can be measured by using 3-single phase voltmeters, instead of a wattmeter.

Simulation:

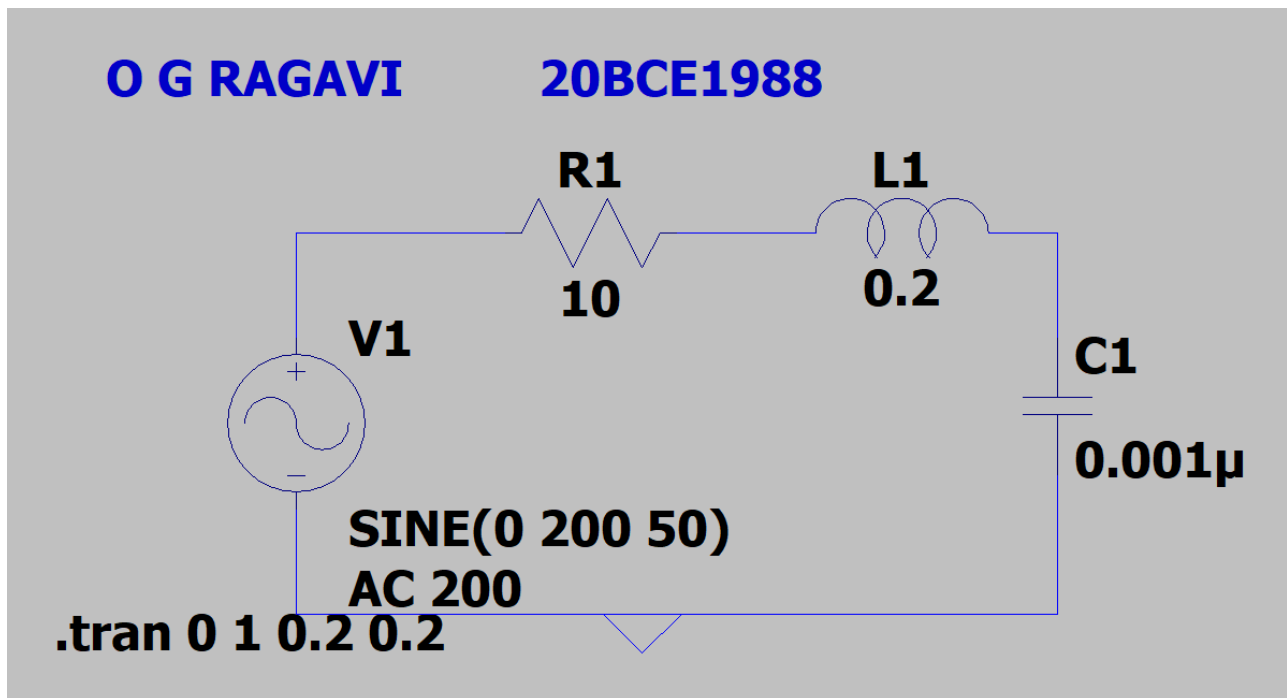

Theoretical Calculation:

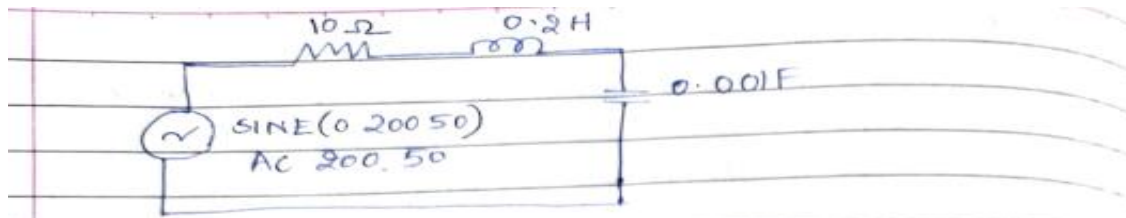

$$f = 50 \text{ Hz}$$

$$\begin{aligned} X_L &= 2\pi fL \\ &= 2\pi(50)(0.2) \\ &= 62.831 \Omega \end{aligned}$$

$$\begin{aligned} X_C &= \frac{1}{\omega C} = \frac{1}{2\pi fC} \\ &= \frac{1}{2\pi(50)(0.001)} \\ &= 3.183 \Omega \end{aligned}$$


$$\begin{aligned} Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{(10)^2 + (62.831 - 3.183)^2} \\ \therefore \boxed{Z &= 60.48 \Omega} \end{aligned}$$

$$\begin{aligned} I &= \frac{V}{Z} = \frac{200}{60.48} = 3.306 \text{ A} \\ \therefore \boxed{I &= 3.306 \text{ A}} \end{aligned}$$

$$\begin{aligned} \phi &= \tan^{-1}\left(\frac{X_L - X_C}{R}\right) \\ &= \tan^{-1}\left(\frac{62.831 - 3.183}{10}\right) \\ \therefore \boxed{\phi &= 80.48^\circ} \end{aligned}$$

$$\begin{aligned} \text{Power} &= VI \cos \phi \\ &= (200)(3.306) \cos(80.48) \\ \therefore \boxed{\text{Power} &= 109.32 \text{ W}} \end{aligned}$$

Simulation results:

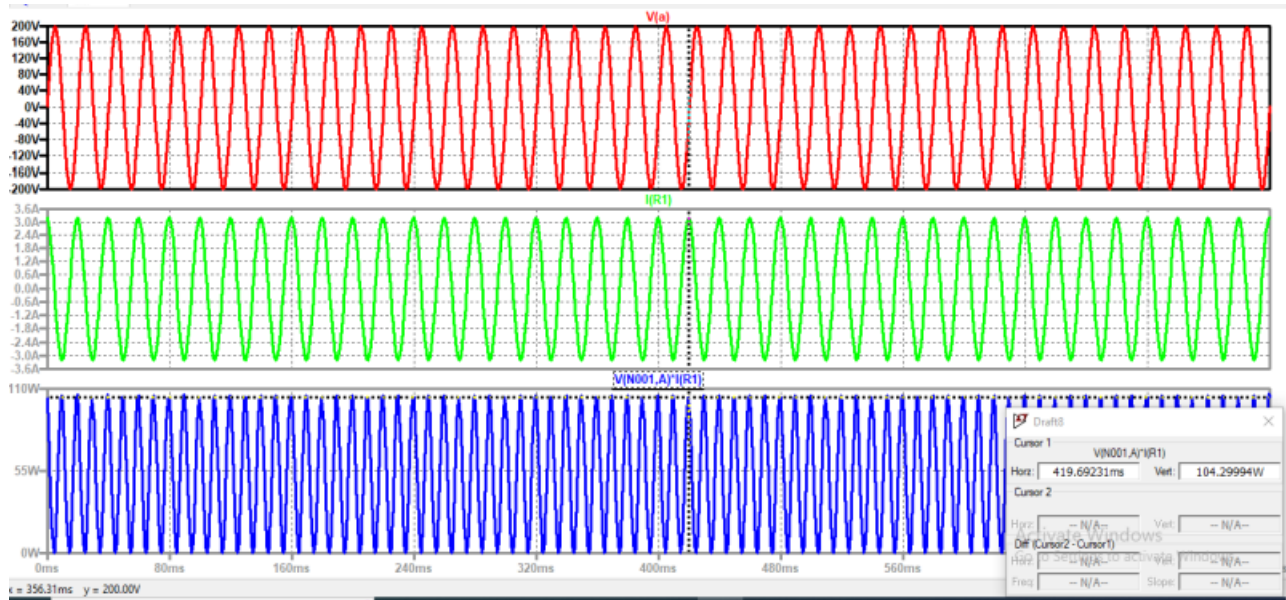

Result:

Thus, The power in single phase ac circuit is measured successfully.

